 



Decoupling Capacitors and PCB Layout: What is Really Important?

Prof Eric Bogatin

Eric.Bogatin@colorado.edu



Spring 2023

 

University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group

1

About the Eric



Eric Bogatin
Prof, University of Colorado, Boulder
Fellow: Teledyne LeCroy
Technical Editor, Signal Integrity Journal

- Physics: BS MIT '76 and PhD U of A Tucson, '80
- Senior management and engineering positions at Bell Labs, Raychem, Sun Micro, Ansys, Interconnect Devices Inc
- Started Bogatin Enterprises in 1992, created the Signal Integrity Academy, acquired by LeCroy in 2011. Teledyne LeCroy Fellow
- Full time Prof, ECEE dept University of Colorado, Boulder, since 2021, teaching signal integrity, PCB design, Capstone Senior Design Lab
- Author: 15 books, including popular textbooks and science fiction novels, monthly columns

2




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



2

Other Resources

 

<https://podcasts.signalintegrityjournal.com>



Special offer for all attendees:

Sign up for complimentary 3-month subscription to the 200 hours of video training on the Signal Integrity Academy
<https://www.bethesignal.com/bogatin/3monthsubscription.php> Use promo code: WEB23

Series of free recorded webinars listed on
www.beTheSignal.com



3



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



3

Major Research Programs of the HSDE Group

- Low-Cost Hands-On **Demonstrations** of SI/PI/EMI Best Design, Simulation, Measurement, Analysis Practices and Pathological Examples (primary audience is course content)
- Low-Cost SI/PI/EMI **Technology Solutions** (primary audience is engineer)
- Improving **Measurement-Simulation Correlation** of Circuits and Interconnects from 1 Hz to 40 GHz
- Low-Cost **Software Defined Instruments**

4



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



4

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

5



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group




5

Design is First About Connectivity

A schematic identifies:

 
- BOM
- Functionality
- Connectivity
- Wires are transparent- no R, no delay



The interconnects live in the wires and the white space of the schematic



 A layout represents the physical design of the interconnects



If the interconnects are transparent, design for performance doesn't apply. It's all about connectivity, DFM, DFR, DFT,...

...but, in almost every design, they are not transparent

***Once connectivity is correct, the only thing interconnects are going to do is screw up the performance
The goal in interconnect design is to minimize how much the interconnects screw things up***

6



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



6

Four Hurdles in PDN Design

- The problem with PDN design is not 1 problem, it is 12 problems
- Identifying the root cause of each problem is hard
- There are 9 orders of magnitude between low current PDNs (1 μA) and high current PDNs (1000 A). One solution cannot apply to all
- There is a lot of “noise” and “legacy code” circulating in the industry about PDN design

7




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



7

 Watch out for the “streetlight effect”: a common origin for PDN design guidelines



The right solution is not always where it's easy to find

8




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



8

 Why PDN Design is so Confusing: It's not just 1 problem and root cause, it's 12



- Self aggression noise
 - From VRM on VRM
 - From Vcc on Vcc (not much on-die capacitance)
 - From Vdd on Vdd (a lot of on-die capacitance)
 - From signals on signals (discontinuities)
- “Pollution” of the board/pkg interconnects
 - From VRM
 - From I/O
 - From core
 - From signals
- Mutual aggressors: cross talk coupling from the PDN
 - To VRM
 - To I/O
 - To core
 - To signals

Best Design Practices Depend on Which PDN Problem You Are Trying to Solve



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



9

9

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

10




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



10

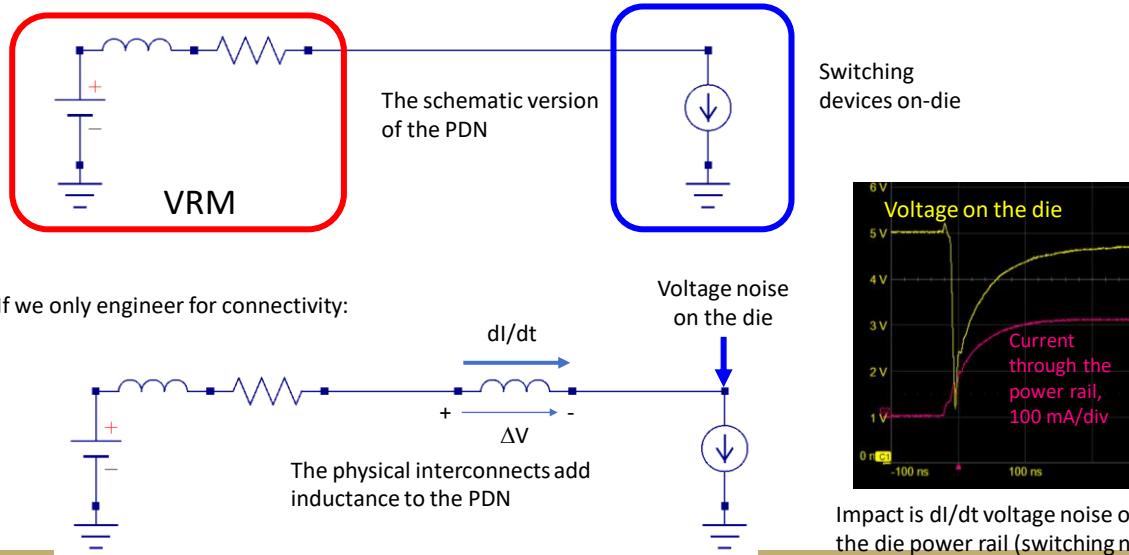The Origin of I/O Switching Noise on the Power Rail




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



11

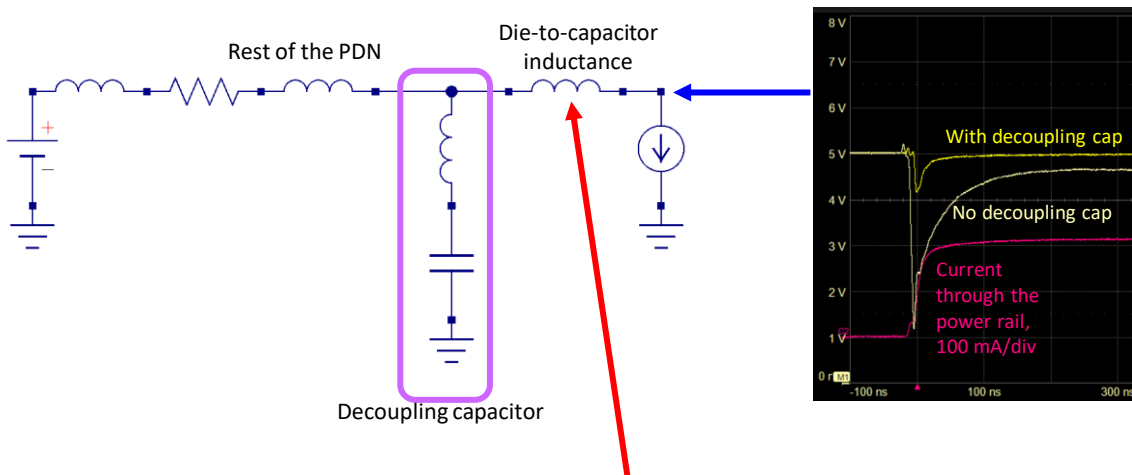Reduce Switching Noise by adding Decoupling Capacitors "Decouples" the IC from the Rest of the PDN Inductance



Switching noise on-die is reduced by reducing the Die-to-capacitor inductance



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



12

12

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

13





University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



13

  An Homage to Bob Pease, “My simulation language is solder”




Slammer circuit

Arduino drives 5% duty cycle pulses, ~ 10 nsec rise time

TIP41C transistor turns on in ~30 nsec

Scope measures voltage across 10 ohm resistor

 Scope measures the voltage on collector (on die)



14



University of Colorado, Boulder, ECEE



High Speed Digital Engineering Group





14

The Origin of I/O Switching Noise on the Power Rail

No
decoupling
capacitor

  

With
decoupling
capacitor

  

15




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



15

How Much Capacitance is Enough?

 


- The purpose of the capacitor is to reduce the inductance the die sees.
- How much capacitance to add?

$$C > \frac{\Delta Q}{\Delta V} = \frac{I \Delta t}{\Delta V} = \frac{0.4 \text{ A} \times 100 \text{ n sec}}{0.1 \text{ V}} = 400 \text{ nF}$$

- To first order, doesn't matter how much larger the capacitor is- just that it is low inductance

 Power rail noise with 1000 uF and 1 uF capacitors



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



16

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

17



University of Colorado, Boulder, ECEE



High Speed Digital Engineering Group



17


A Circuit Board Experiment

with my student Ameya Ramadurgakar

 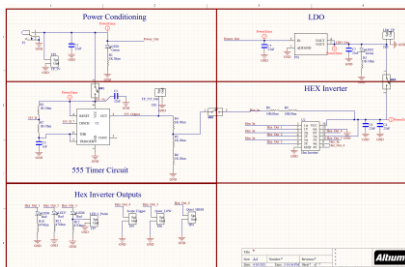

Features: 555 timer at 500 Hz

 Drives inputs to Hex inverter
 Outputs 1, 2, 3 drive 50 ohms and RED LED (25 mA each)
 Output 4 drives trigger to scope
 Output 5 is pegged low (quiet low, on die)
 Output 6 is pegged HI (quiet High, on die)



18



University of Colorado, Boulder, ECEE




High Speed Digital Engineering Group



18

Three Identical Schematics, Different Layouts

   Identical boards. Just differ by placement of the 2 decoupling capacitors for the hex inverter



Boards designed by Ameya Ramadurgakar

Rule #9: what do we expect?

19





University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



19

  Important Design Principle for Prototypes: Design for Test and Bring Up with 10x Probe Test Points



20




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



20

Really Bad Routing

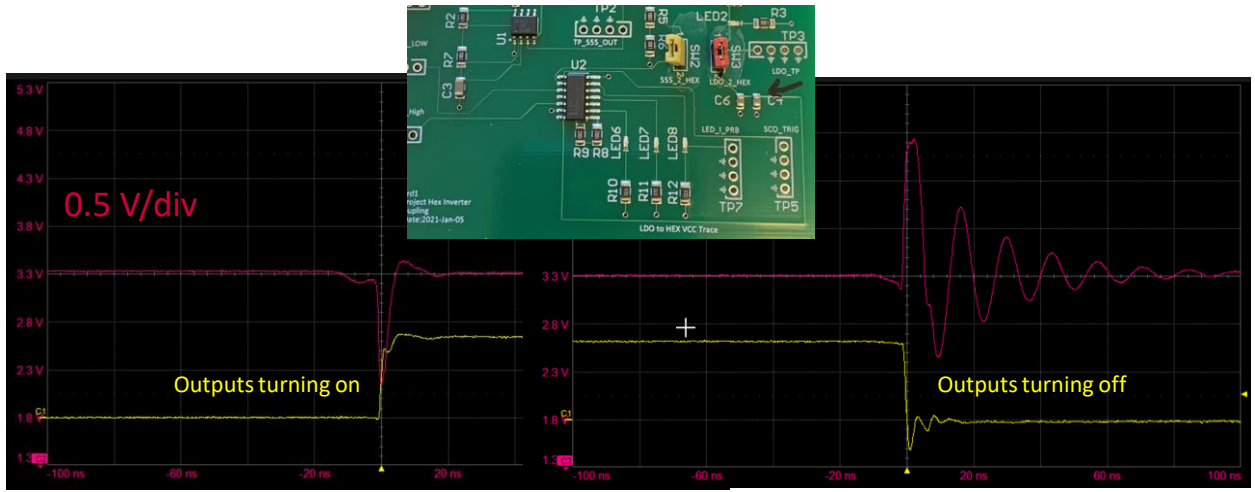

21




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



21

Fair Routing

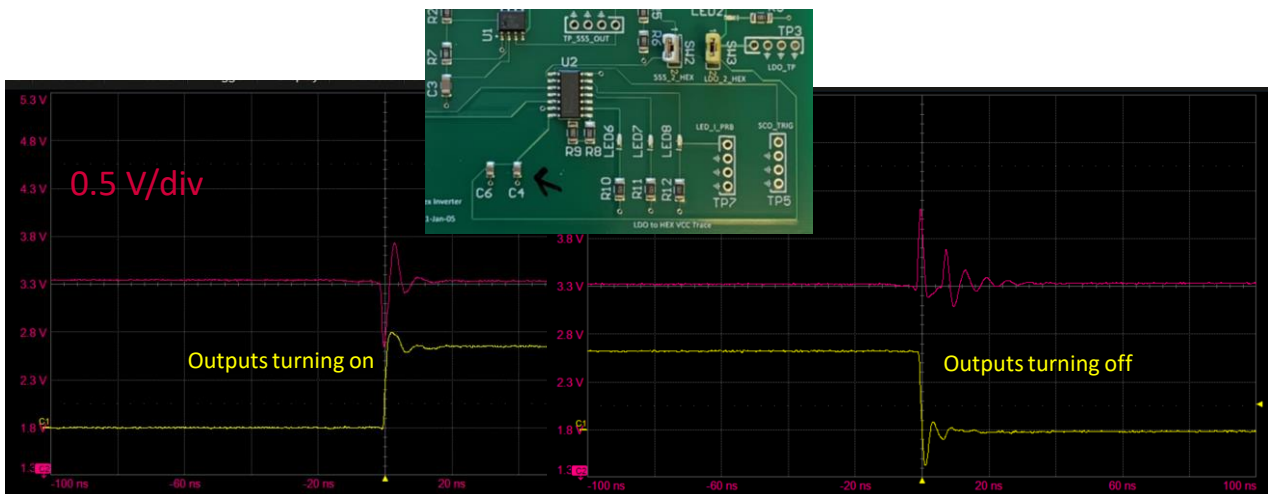

22




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



22

Best Routing

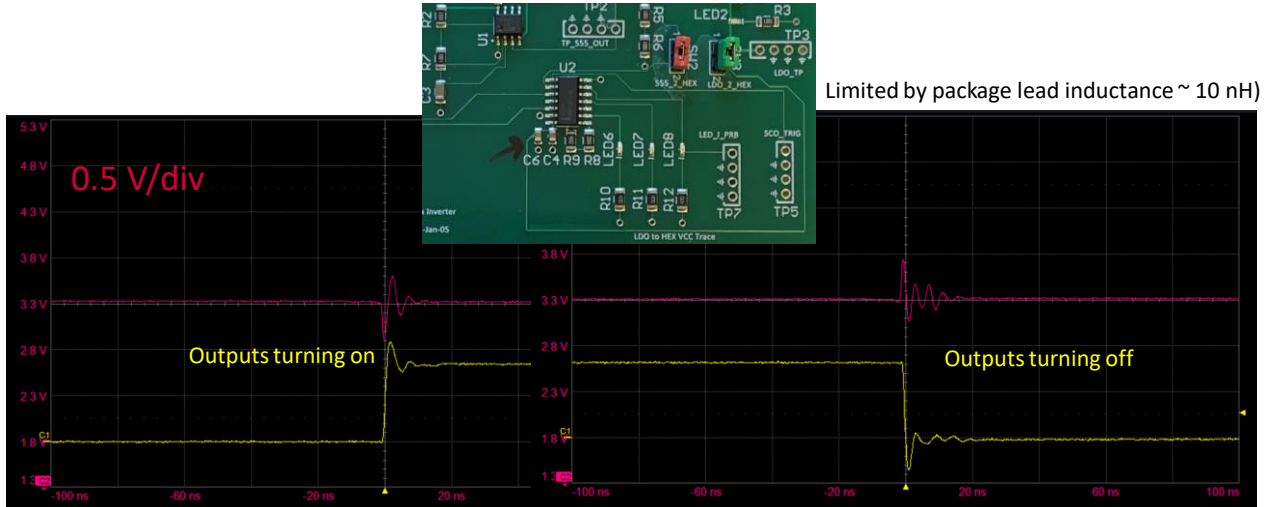

23



23

How the Decoupling Capacitors are Placed, Matters



24



24

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

25



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



25

Historical Driving Force in Reducing Switching Noise: use three different value decoupling capacitors: 10 μF , 1 μF , 0.1 μF


- How to achieve low inductance?

<https://www.signalintegrityjournal.com/articles/1589-the-myth-of-three-capacitor-values>



Historically:

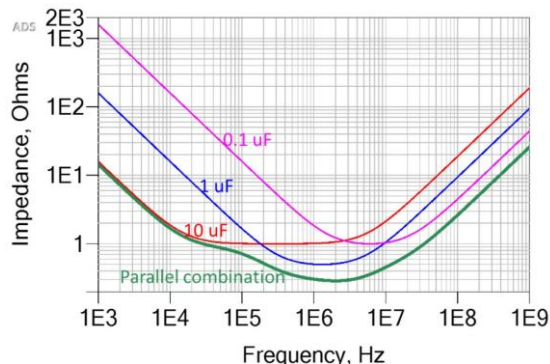- Smaller capacitance value capacitors were smaller physical size and lower inductance: "High frequency capacitors"
- Use small size capacitors to get low inductance. Add larger size capacitors to get more capacitance.
- The origin of the recommendation: Use three capacitors in parallel: 10 μF , 1 μF , 0.1 μF



26




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



26

A Common Design Guideline for 50 Years

 


University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



27

The Reality Today

 

<https://www.signalintegrityjournal.com/articles/1589-the-myth-of-three-capacitor-values>

The reality:


- High frequency impedance is not about the capacitance, it is about the lead loop inductance
- A "high frequency capacitor" just has low loop inductance

Three different value capacitors is legacy code.

Use 1 capacitor, use 3 capacitors, the same value, 3 different values:

- ✓ Your design may work
- ✓ Your design may not work
- ✓ Your design may work in spite of your choice, not because of it
- Either "test in" design or do detailed analysis

➤ **Low inductance is the key**

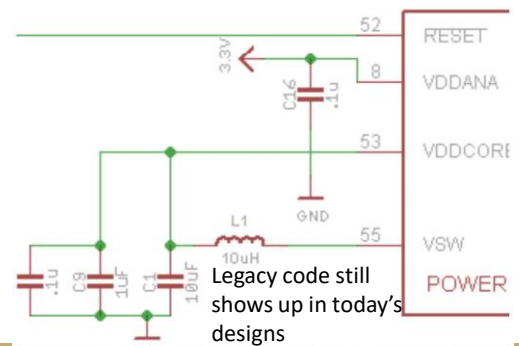

University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



28

Agenda

- Challenges in PDN design
- One example: rail collapse for I/O switching
- An homage to Bob Pease
- So what? good and not so good PCB layout strategies
- Legacy Code
- Final recommendations

29




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



29

 Why PDN Design is so Confusing: It's not just 1 problem and root cause, it's 12



- Self aggression noise
 - From VRM on VRM
 - From Vcc on Vcc (not much on-die capacitance)
 - From Vdd on Vdd (a lot of on-die capacitance)
 - From signals on signals (discontinuities)
- “Pollution” of the board/pkg interconnects
 - From VRM
 - From I/O
 - From core
 - From signals
- Mutual aggressors: cross talk coupling from the PDN
 - To VRM
 - To I/O
 - To core
 - To signals

Best Design Practices Depend on Which PDN Problem You Are Trying to Solve



University of Colorado, Boulder, ECEE


High Speed Digital Engineering Group



30

30

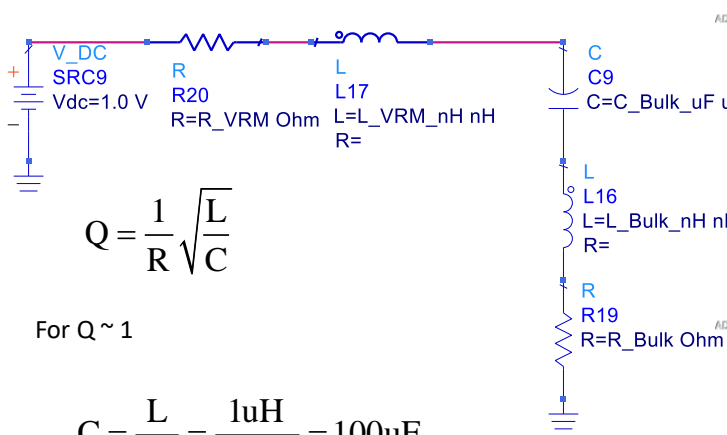
Selecting the Bulk Decoupling Capacitor is about Managing the Parallel Resonance with the VRM Inductance




$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

For $Q \sim 1$

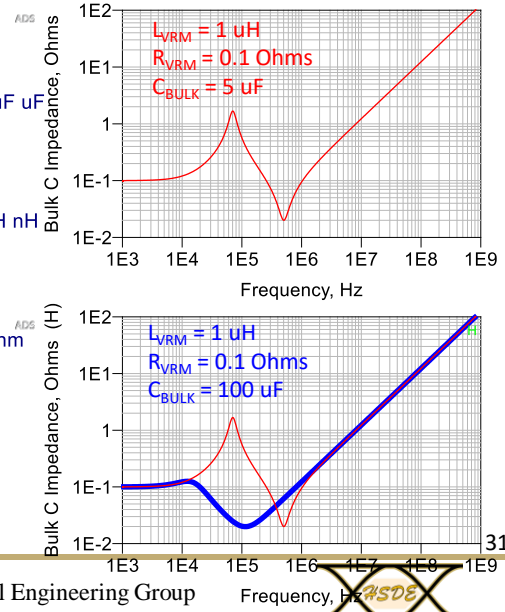
$$C = \frac{L}{R^2} = \frac{1\mu\text{H}}{(0.1)^2} = 100\mu\text{F}$$



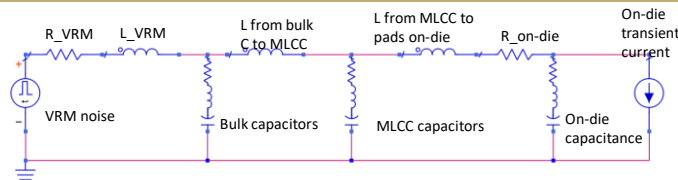PDN Design for the Core Rail is Dominated by Managing the Bandini Mountain



 Managing PDN impedance is about managing the peaks (parallel resonances)



Biggest parallel resonance: between the on-die capacitance and the package inductance including the ESL of the MLCC capacitors



The "Bandini Mountain"

- Steve Weir



Luck and Hope Should Not be Part of the Design Process



The faster you go, the less luck you seem to have

There is no substitute for applying good engineering principles



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



33

Conclusion

- Interconnects will only add noise to your product
- Reduce noise by identifying potential problems and designing them out
- Base your designs on the root cause of the potential problems
- Turn the root cause into design guidelines
- There is no substitute to good engineering principles

34




University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group



34

Other Resources

 

<https://podcasts.signalintegrityjournal.com>



Special offer for all attendees:

Sign up for complimentary 3-month subscription to the 200 hours of video training on the Signal Integrity Academy
<https://www.bethesignal.com/bogatin/3monthsubscription.php> Use promo code: WEB23

Series of free recorded webinars listed on
www.beTheSignal.com



35



University of Colorado, Boulder, ECEE

High Speed Digital Engineering Group

